


# 90th International Conference of Doble Clients

March 26–31, 2023 | Boston, Massachusetts USA

## Winding Resistance Issue During Transformer Bushings Replacement

Andrew Stenabaugh – Ontario Power Generation

Ed teNyenhuis – Hitachi Energy

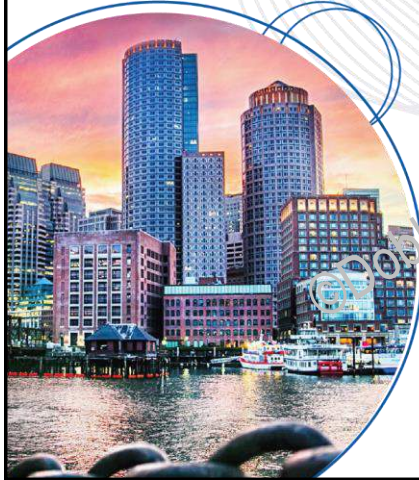

1

## Confidential Notice



Doble Engineering (Doble) hereby grants the recipient (you) the right to retain this presentation and materials included within (the Presentation) for private reference. No other rights, title, or interest, including, but not limited to, the rights to copy, make use of, distribute, transmit, display or perform in public (or to third parties), edit, translate, or reformat any portion of the Presentation are hereby or otherwise granted and shall remain expressly reserved by Doble. You acknowledge and agree that such limited license is expressly conditioned upon your acceptance of the terms herein. You further agree that, in the event of your breach, Doble will suffer irreparable damage and injury for which there is no adequate remedy at law. As such, Doble, in addition to any other rights and remedies available, shall be entitled to seek injunction by a tribunal of competent jurisdiction restricting you from committing or continuing any breach of these terms.

©2023 Doble Engineering Company. All Rights Reserved.

2

## Contents



- Introduction
- Site & project background
- Winding Resistance Problem
- Investigation
- Winding Resistance issue modeling
- Conclusions


©2023 Doble Engineering Company. All Rights Reserved.

3
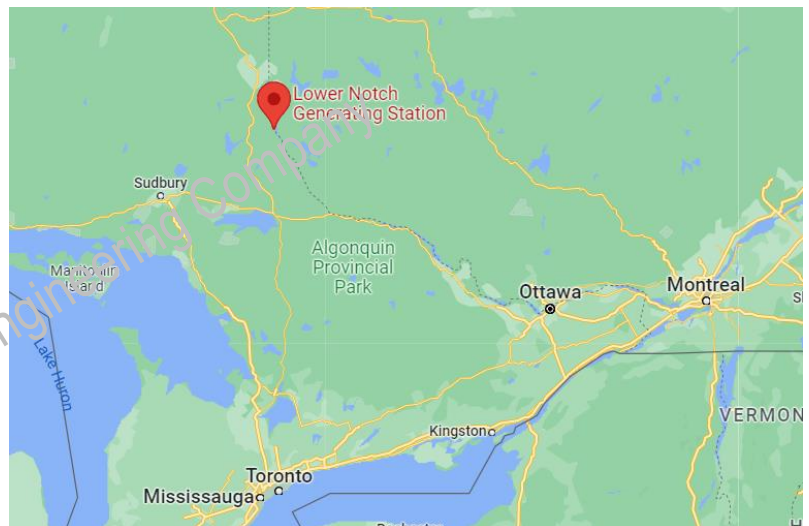
## Ontario Power Generation – Lower Notch GS



- Located on Montreal River (35km from Cobalt, Ontario)
- Into service in 1971




©2023 Doble Engineering Company. All Rights Reserved.

4
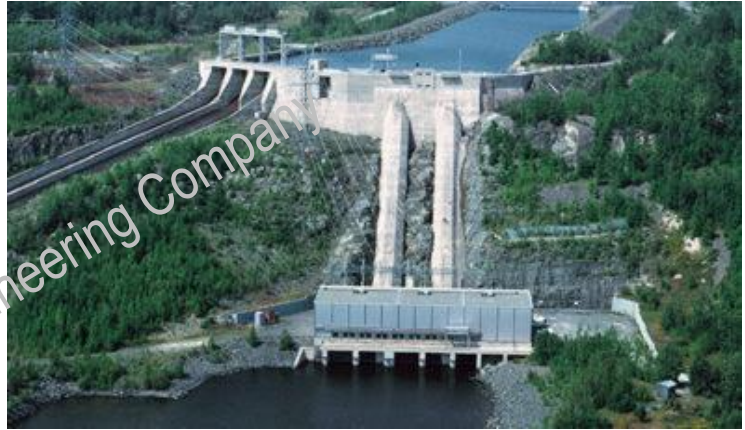
## Ontario Power Generation – Lower Notch GS



- Maximum station capacity of 274.2MW
- 2 X 138MVA, 13.8kV generators, G1 and G2
- 2 X 140MVA, 13.4kV-230kV, 3 phase generator step up transformers - T1 and T2



©2023 Doble Engineering Company. All Rights Reserved.

5

## Ontario Power Generation – Lower Notch GS



- Transformers T1 and T2 installed in 2000



©2023 Doble Engineering Company. All Rights Reserved.

6

## Connection to Generator



- LV connection via iso-phase bus duct to generator



©2023 Doble Engineering Company. All Rights Reserved.

7

## Transformer Maintenance



- Yearly - oil analysis, visual inspections of critical components and deluge system testing
- 6 year - complete inspection of tank, bushings, tap changer, lightning arrestors, radiators, gauges, gas relays, auxiliary devices & electrical testing (insulation resistance, power factor, micro-ohm and windings ratio testing on the in-service tap)

©2023 Doble Engineering Company. All Rights Reserved.

8

## LV Bushing Replacement Project



- Repair of leaks on the LV and HV bushing stacks required
- Required replacement of LV bushings, LV bushing gaskets, HV bushing gaskets and some valves
- Project initiated to perform this scope along with complete electrical testing
- Required complete draining of the transformers
- T1 work done in 2021, T2 work done in 2018

©2023 Doble Engineering Company. All Rights Reserved.

9

## Winding Resistance Issue on T1 Unit



- Winding resistance measured before and after the LV bushing replacement – 22% increase in 1 phase and 6% increase in the other 2 phases
- T2 unit had no change in resistance



	all milli ohms @85C	X1 - X2	X2 - X3	X3 - X1	% Difference between Phases
1	FAT	2.580	2.580	2.590	0.39%
2	Pre Test	2.554	2.571	2.549	0.87%
3	First Measurement	2.695	3.138	2.681	16.08%
4	% Change	6%	22%	5%	

©2023 Doble Engineering Company. All Rights Reserved.

10

10

## Measured Winding Resistance Limits



- IEEE Standard C57-152-2013 “IEEE Guide for Diagnostic Field Testing of Fluid-Filled Power Transformers, Regulators, and Reactors”
- Recommended that winding resistance measurements in the field should be within 2% of other phases or the original factory test report, but no more than 5% higher


©2023 Doble Engineering Company. All Rights Reserved.

11
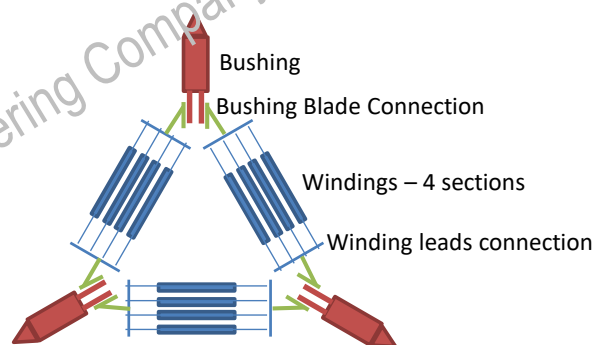
## LV Delta Connection



- LV delta connection made at bushings
- 4 large leads for each winding phase group



©2023 Doble Engineering Company. All Rights Reserved.

12

12

## Investigation



1. Remeasured with different test equipment - Same result
2. Measured resistance of bushings only – Very low, not the issue
3. Disconnected bushings and measured without bushings in the circuit – Same result
4. Broke the delta connection and measured each winding phase  
Measured high result on winding 2 phase only
5. Measured 4 winding leads on bad phase – OK
6. Disconnected 4 leads at the copper plates - Issue found with the copper plate connecting the winding lead

©2023 Doble Engineering Company. All Rights Reserved.


13

13
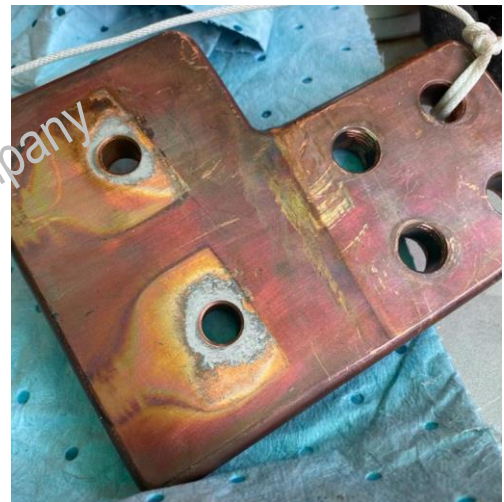
## Investigation Continued



- Found heavy surface contamination or build-up on copper plate
- Removed the copper connector plate and cleaned thoroughly
- Reconnected and winding resistance was good



©2023 Doble Engineering Company. All Rights Reserved.

14

14

## Copper Plate – Before and After Cleaning



©2023 Doble Engineering Company. All Rights Reserved.

15

## Winding Resistance Measurement



- Final measured values were close to FAT and within IEEE recommended limits

	all milli ohms @85C	X1 - X2	X2 - X3	X3 - X1	% Difference between Phases
1	FAT	2.556	2.586	2.598	0.48%
2	Pre Test	2.554	2.571	2.549	0.87%
3	Final test	2.577	2.683	2.578	4.05%
4	% Change	1%	4%	1%	

©2023 Doble Engineering Company. All Rights Reserved.


16


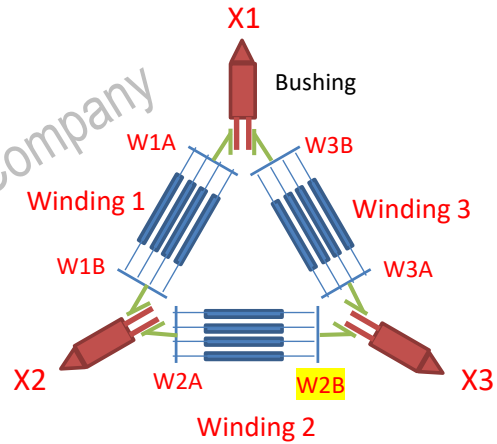
# Location of Copper Plate Issue – see W2B



- W1A = Winding 1 Top Leads Connection Plate
- W1B = Winding 1 Bottom Leads Connection Plate
- W2A = Winding 2 Top Leads Connection Plate
- W2B = Winding 2 Bottom Leads Connection Plate
- W3A = Winding 3 Top Leads Connection Plate
- W3B = Winding 3 Bottom Leads Connection Plate



©Doble Engineering Company. All Rights Reserved.

# Modeling of High Resistance



Normal Case		Bad W2B Connection	
All values in milli ohms @85C		All values in milli ohms @85C	
Winding 1 Path		Winding 1 Path	
W1A	0.05	W1A	0.05
Winding Sections	3.705	Winding Sections	3.705
W1B	0.05	W1B	0.05
<b>Total</b>	<b>3.805</b>	<b>Total</b>	<b>3.805</b>
Winding 2 Path		Winding 2 Path	
W2A	0.05	W2A	0.05
Winding Sections	3.705	Winding Sections	3.705
W2B	0.05	<b>W2B</b>	<b>1.4</b>
<b>Total</b>	<b>3.805</b>	<b>Total</b>	<b>5.155</b>
Winding 3 Path		Winding 3 Path	
W3A	0.05	W3A	0.05
Winding Sections	3.735	Winding Sections	3.735
W3B	0.05	W3B	0.05
<b>Total</b>	<b>3.835</b>	<b>Total</b>	<b>3.835</b>

©2023 Doble Engineering Company. All Rights Reserved.

## Modeling of High Resistance



X1 - X2 Measurement			X1 - X2 Measurement	
Short path (Winding 1)	3.805		Short path (Winding 1)	3.805
Long path (Winding 2 + Winding 3)	7.64		Long path (Winding 2 + Winding 3)	8.99
Bushing X1	0.02		Bushing X1	0.02
Bushing X2	0.02		Bushing X2	0.02
<b>Total X1 - X2 calculated</b>	<b>2.580</b>		<b>Total X1 - X2 calculated</b>	<b>2.713</b>
FAT Measured	2.580		<b>Site Measured</b>	<b>2.695</b>
X2 - X3 Measurement			X2 - X3 Measurement	
Short path (Winding 2)	3.805		Short path (Winding 2)	5.155
Long path (Winding 3 + Winding 1)	7.64		Long path (Winding 3 + Winding 1)	7.64
Bushing X2	0.02		Bushing X2	0.02
Bushing X3	0.02		Bushing X3	0.02
<b>Total X2 - X3 Calculated</b>	<b>2.580</b>		<b>Total X2 - X3 Calculated</b>	<b>3.118</b>
FAT Measured	2.580		<b>Site Measured</b>	<b>3.138</b>
X3 - X1 Measurement			X3 - X1 Measurement	
Short path (Winding 3)	3.835		Short path (Winding 3)	3.835
Long path (Winding 1 + Winding 2)	7.61		Long path (Winding 1 + Winding 2)	8.96
Bushing X3	0.02		Bushing X3	0.02
Bushing X1	0.02		Bushing X1	0.02
<b>Total X3 - X1 Calculated</b>	<b>2.590</b>		<b>Total X3 - X1 Calculated</b>	<b>2.726</b>
FAT Measured	2.590		<b>Site Measured</b>	<b>2.681</b>

©2023 Doble Engineering Company. All Rights Reserved.

19

## Discussion of High Resistance



- Delta winding resistance connection (bushing to bushing) has 2 paths (short path through 1 winding and longer path through the other 2 windings in series)
- Estimated 1.4 milli-ohms of added resistance at the copper plate (each winding is 3.7 milli-ohms)
- Very large added resistance could be 17kW ( $I^2R$ )
- Likely this would have overheated and gassed in service

©2023 Doble Engineering Company. All Rights Reserved.

20

## Discussion of High Resistance



- Problem with copper plate most likely occurred when it was moved slightly to align with the bushing blade
- Slight movement seems to have disturbed the 4 lead connectors on the copper plate
- Corrosion on the copper plate between the connector and the copper plate caused the contact resistance to increase significantly
- Not clear why there was a high contact resistance

©2023 Doble Engineering Company. All Rights Reserved.

21

## Summary / Conclusions



- Even though the bad connection was not part of the bushing changeout, it was disturbed by physical movement
- Calculations later showed the added resistance was in the order of 35% of the winding resistance - would have caused very high loss and heating in this small area if not fixed
- Delta connection made the winding resistance increase appear to be less severe due the parallel phase paths softening the measured phase to phase increase
- Case demonstrates
  - Importance of the winding resistance measurement
  - Winding resistance differences should be investigated to resolution
  - Subtleties of understanding a high winding resistance in a delta connection

©2023 Doble Engineering Company. All Rights Reserved.

22

22